

ELECTRIC CIRCUITS: TEACHER GUIDE

Twelve 50-minute lessons, written for students with **no prior knowledge of electricity**. Each lesson has a matching section in the student workbook and a mission on the companion website.

HOW THE THREE RESOURCES FIT TOGETHER

RESOURCE	USED FOR
Student workbook	One booklet per lesson (12 pt text, wide writing lines), each with its toolkit, key words and quick answers, plus a Unit review booklet with the static electricity page (Physics only) and progress tracker. Every lesson: explanations, worked examples, graded practice, lab records, an exam question and a revision box. It is the students' classwork book and their revision guide.
Answer edition	Same pages and page numbers as each booklet, with answers in blue. For marking, and for release to students for self-marking if you choose.
Companion website	panphy.app/gcsephy/year10phy/unit01/: homework and revision. Missions carry more questions with hints and worked answers; the Exam Zone is for the end of the unit.
Virtual labs, practicals	Lessons 2–4 use the Virtual Labs worksheet (PhET) for the full investigation; the workbook holds a short record. Lab 3 plots current against p.d., as AQA does. Lessons 5, 7 and 9 are the required practicals: the workbook is the lab sheet, and the website has a matching page for each.

DESIGN PRINCIPLES

- **Concrete before abstract.** Lesson 1 builds real circuits and teaches symbols and drawing rules before any quantity is measured. The voltmeter appears only when students know what p.d. is (Lesson 3).
- **One new idea at a time.** Current, p.d. and resistance get a lesson each, each with a model (bike chain, delivery vans, collisions) and its limitation. Common misconceptions appear as student claims (Mia, Leo, Ava) to correct.
- **Worked example → your turn → faded practice.** Calculation questions go from a full frame (Equation, Substitute, Answer) to no frame to a challenge.
- **Retrieval every lesson.** 'Do now' questions revisit earlier lessons; 'Revise it' gives cover-and-answer questions with quick answers at the back.
- **Equations are still learned.** AQA provides the full Physics Equations Sheet in every paper, confirmed for 2027 and from 2028 onwards. It does not include $R_{\text{total}} = R_1 + R_2$, and students who know the equations work faster, so the booklet still teaches recall.

SEQUENCE

#	LESSON	COMPANION WEBSITE
1	Complete circuits and symbols What a circuit needs, circuit symbols and drawing rules, measuring current	Mission 1: Build & measure
2	Current and charge Current as a rate of flow of charge, $Q = I t$, current is not used up	Mission 2: Charge on the move
3	Potential difference p.d. as energy per coulomb, voltmeters, $E = Q V$, p.d.s add in series	Mission 3: Energy per coulomb
4	Resistance and $V = I R$ Resistance, $V = I R$, ohmic conductors, why heating raises resistance	Mission 4: Resistance & $V = I R$
5	Resistance of a wire REQUIRED PRACTICAL Required practical: how the length of a wire affects its resistance	Required practical: Resistance
6	Series and parallel circuits Current, p.d. and resistance rules for series and parallel circuits	Mission 5: Series & parallel
7	Resistors in series and parallel REQUIRED PRACTICAL Required practical: measure total resistance of two resistors in series and in parallel	Required practical: Resistance (Part B)
8	I–V graphs I–V graphs of a fixed resistor, filament lamp and diode	Mission 6: I–V characteristics
9	Investigating I–V characteristics REQUIRED PRACTICAL Required practical: measure the I–V characteristics of a resistor, lamp and diode	Required practical: I–V characteristics
10	Thermistors, LDRs and sensors How thermistors and LDRs respond to temperature and light, and sensor circuits	Mission 6: Thermistor and LDR
11	Power and energy transfer Power, $E = P t$, $P = V I$, $P = I^2 R$, energy transfers in appliances	Mission 7: Power & the National Grid

#	LESSON	COMPANION WEBSITE
12	Mains, safety and the National Grid ac and dc, 230 V 50 Hz mains, three-core cable, earthing, the National Grid	Missions 7 and 8

COMPLETE CIRCUITS AND SYMBOLS

AQA Combined 6.2.1.1; Physics 4.2.1.1; 50 minutes

BIG QUESTION Your torch won't switch on. The bulb is fine and the batteries are new. What could be wrong?

STUDENTS WILL BE ABLE TO

- explain why a lamp only lights in a complete loop
- recognise and draw standard circuit symbols
- turn a real circuit into a neat circuit diagram
- connect an ammeter in series to measure current

WHY THIS LESSON, HERE

Students start with no formal knowledge. Before any quantity or equation, they need a working idea of a circuit and the vocabulary to draw one. The old Lesson 1 asked for six symbols that were never taught; this lesson teaches them explicitly, from real apparatus to symbol to diagram.

PREPARATION AND EQUIPMENT

Per pair: 1.5 V cell (or 2 × AA in a holder), lamp in holder, switch, 4 leads, ammeter (0–1 A). One broken torch for the hook (loose battery contact). Optional: a bike or a chain loop to show the model.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Hook + starting point	Show the torch that won't work. Students answer the three 'What do you already think?' boxes. Collect ideas; do not correct yet.
6–16	Build first	Pairs build cell + switch + lamp from the picture, before any symbols. Ask: what did every working circuit have in common? Draw out 'complete loop'.
16–26	Picture → symbol → diagram	Teach the solid row of symbols and the drawing rules. Model drawing the pairs' own circuit on the board with a ruler.
26–32	Ammeter	Add the ammeter in series; read it. Name 'current' and 'series' only. Charge, $Q = I t$ and p.d. wait until Lessons 2–3.
32–44	Try it	Questions 1–5. Circulate on Q4 (spot the mistakes) and Q5 (draw it): these show whether the drawing rules have landed.
44–50	Exam corner	Q7 as a hinge: check symbols, loop and ammeter placement. Q6 (torch detective) for homework if needed.



Hinge check. Show circuit C from Q3. 'Will the lamp light?' If more than a few say yes, reteach 'a gap anywhere stops the current everywhere' before moving on.

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
The cell 'fills up' the wire with electricity, which travels from the cell to the lamp.	Use the bike-chain model: the charges are already in the wire and all move together.
Current is used up by the lamp.	Plant the idea with two ammeters now; test it properly in Lesson 2.
Symbols can go anywhere near the wire.	Q4 makes the rule explicit: the wire must go into the symbol.

SUPPORT

Give out a symbol card set to match with real components before drawing. Allow tracing the symbol bank for Q2.

STRETCH

Draw a circuit with two lamps and a switch that controls only one of them (early preview of parallel).

Homework: Companion website, Mission 1: notes and all five questions. Workbook: Revise it.

CURRENT AND CHARGE

AQA Combined 6.2.1.2; Physics 4.2.1.2; Virtual Lab 1; 50 minutes

BIG QUESTION Flick a switch and the lamp lights instantly, yet each electron drifts through the wire slower than a snail. How can both be true?

STUDENTS WILL BE ABLE TO

- describe current as the rate of flow of charge
- use $Q = I t$, with time in seconds
- explain why the current is the same everywhere in a single loop

WHY THIS LESSON, HERE

Current is defined as a rate before students calculate with it. The model (bike chain, then ticket barrier) explains the instant switch-on puzzle and why current is conserved, so $Q = I t$ is attached to meaning rather than a triangle.

PREPARATION AND EQUIPMENT

Computers or tablets with PhET Circuit Construction Kit: DC (Lab). Virtual Labs worksheet pp. 3–6 for pairs who finish. Optional: a real series loop with two ammeters.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now	Retrieval from Lesson 1. Then pose the big question and take predictions.
6–18	Learn	Free electrons, coulombs, current as a rate (ticket barrier). Model the worked example; students do 'Your turn' on mini whiteboards.
18–32	Virtual Lab 1	Pairs measure current at three points, then change R. Record in the Lab box. Ask: 'Where did the current go?'
32–44	Try it	Q1–Q5 in order: the calculation questions fade from full frame to no frame. Q6 is the challenge. Q7 is the misconception check.
44–50	Exam corner	Questions 10–11. Peer mark using the tip: time conversion, unit.



Hinge check. Q2 (0.60 A means...). Anyone choosing '0.60 C in the circuit' needs the ticket-barrier model again.

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
Current is used up.	Virtual Lab 1 plus Q7. Language: charge goes round; energy is transferred.
Minutes go straight into $Q = I t$.	Every supported frame has a 'Convert' row first.
Electrons flow from + to –.	Show both arrows on one diagram; exam diagrams use conventional current.

SUPPORT

Keep the frames; give a units card (C, A, s).

STRETCH

How many electrons pass in 1 s at 1 A? ($\approx 6 \times 10^{18}$.) Explain why a bigger current does not need faster-moving electrons in a thicker wire.

Homework: Mission 2 practice questions (with worked answers). Finish Virtual Lab 1 pp. 4–6 if not done.

POTENTIAL DIFFERENCE

AQA Combined 6.2.1.3, 6.2.4.2; Physics 4.2.1.3, 4.2.4.2; Virtual Lab 2; 50 minutes

BIG QUESTION An AA battery says 1.5 V. A car battery says 12 V. What is that number actually telling you?

STUDENTS WILL BE ABLE TO

- explain p.d. as the energy transferred per coulomb
- connect a voltmeter in parallel across a component
- use $E = QV$
- explain why the p.d.s in a loop add up to the supply p.d.

WHY THIS LESSON, HERE

p.d. is the hardest idea in the unit. It is taught as energy per coulomb, with a model (delivery vans) and an explicit contrast with current, before it is used in $V = IR$. The voltmeter is introduced here, when students know what it measures.

PREPARATION AND EQUIPMENT

PhET (Lab) and Virtual Labs worksheet pp. 7–10. Real demo: 6 V supply, two lamps in series, two voltmeters.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now	Retrieval: current, $Q = It$, current not used up.
6–18	Learn	Delivery-van model; $1\text{ V} = 1\text{ J/C}$. Worked example and Your turn. Voltmeter in parallel: say ‘across’.
18–30	Virtual Lab 2	Measure resistor p.d. at 3, 6, 9 V; calculate E for 2 C. Add a second resistor and test ‘p.d.s add up’.
30–43	Try it	Q1 (meter placement) as a class hinge first, then Q2–Q6.
43–50	Exam corner	Questions 9–10; model a two-idea explanation (joules + per coulomb).



Hinge check. Q1: which circuit measures the p.d. across the lamp? Students who pick B are still thinking of meters as ‘in the loop’.

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
Voltage is the speed or ‘strength’ of the current.	Q6 (Leo). Energy per coulomb, not speed.
p.d. ‘at’ a point.	A p.d. is always between two points; insist on ‘across’.
Voltage is used up so current falls.	Energy is transferred; current stays the same (link to Lesson 2).

SUPPORT

Current vs p.d. comparison table on a card; sentence starter ‘___ J of energy is transferred for every ___’.

STRETCH

A 9 V battery drives 0.50 A for 40 s. Find the charge and then the energy (two-step).

Homework: Mission 3 practice questions. Revise it box.

RESISTANCE AND $V = IR$

AQA Combined 6.2.1.3–6.2.1.4; Physics 4.2.1.3–4.2.1.4; Virtual Lab 3; 50 minutes

BIG QUESTION A dimmer switch makes a lamp glow less brightly. What is it actually changing?**STUDENTS WILL BE ABLE TO**

- describe resistance and its unit, the ohm (Ω)
- use $V = IR$, including mA and k Ω
- recognise an ohmic conductor from data or a graph
- explain why heating a metal increases its resistance

WHY THIS LESSON, HERE

$V = IR$ now joins current and p.d., which students understand separately. The particle picture of resistance (collisions with ions) is taught here so that the lamp curve in Lesson 8 is a consequence, not a new fact.

PREPARATION AND EQUIPMENT

PhET (Lab), Virtual Labs pp. 11–14. Demo: dimmer (variable resistor) with a lamp.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now	Retrieval: p.d. meaning, voltmeter, p.d.s add up.
6–18	Learn	Resistance as opposition; two circuits at 6 V. $V = IR$ with both worked examples (the second includes mA).
18–30	Virtual Lab 3	Change battery only; $V \div I$ stays at 10 Ω . Note the axis convention box.
30–44	Try it	Q1–Q4 (fading calculation support), Q5 table + graph, Q6 temperature.
44–50	Exam corner	Questions 9–10.

**Hinge check.** Q1: same battery, 10 Ω vs 30 Ω . Tests the direction of the relationship before any number work.**MISCONCEPTIONS TO EXPECT**

STUDENTS MAY THINK...	ADDRESS IT BY...
Bigger resistance $\rightarrow$ bigger current ('more resistor, more electricity').	Two circuits side by side at the same p.d.
Any straight line means ohmic.	Straight line through the origin; check $V \div I$.
mA used as A.	Worked example 2 converts explicitly.

SUPPORT

Rearranging help: the companion website's equation triangles (optional). Keep frames.

STRETCH

Mission 4 question 5 (electrons and ions). Why does a lamp's resistance rise but a resistor's not (in normal use)?

Homework: Mission 4 practice questions.

RESISTANCE OF A WIRE

AQA Combined RP 15; Physics RP 3; Part A; 50 minutes

BIG QUESTION If you double the length of a wire, what happens to its resistance?**STUDENTS WILL BE ABLE TO**

- set up a circuit to find resistance from V and I
- identify and control the variables
- record, process and graph results
- write a conclusion using evidence

WHY THIS LESSON, HERE

The first required practical. Students can now draw the circuit, place both meters and calculate R , so the practical is about method, variables and evidence rather than new content.

PREPARATION AND EQUIPMENT

Per group: low-voltage dc supply ($\approx 2\text{ V}$), switch, ammeter, voltmeter, 1.1 m of constantan/nichrome wire (e.g. 0.3 mm) taped to a metre ruler, two crocodile clips, leads. Website practical page (Resistance, Part A) for reference.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now	Retrieval: $R = V \div I$, heating, meter symbols.
6–14	Plan	Complete the variables table (Q1). Walk through the circuit and safety. Stress switch-off between readings.
14–34	Practical	Ten lengths, 10–100 cm. Readings in the Results table. Repeat any anomaly immediately.
34–44	Process	Calculate R , plot the graph, line of best fit. Graphs can be finished for homework.
44–50	Analyse	Q4 and Q5 (pattern and prediction). Exam corner Q9 can be set as homework.



Hinge check. Why switch off between readings? (Q7.) If students answer 'to save the battery', reteach heating $\rightarrow$ resistance.

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
'Measure resistance with the voltmeter.'	Resistance is calculated from V and I .
Line of best fit = dot-to-dot.	Model a single straight line through the origin region, ignoring the anomaly.
Increasing length reduces current, so 'current is the DV'.	The DV is R (calculated).

SUPPORT

The length axis is pre-scaled; give a resistance scale (e.g. 2 cm for $1\ \Omega$) and a partially completed example table.

STRETCH

Q8: explain a non-zero intercept (zero error at the clip).

Homework: Finish graph. Exam corner six-mark method. Mission 4 questions 6–9 (measuring resistance and the wire practical).

SERIES AND PARALLEL CIRCUITS

AQA Combined 6.2.2; Physics 4.2.2; 50 minutes

BIG QUESTION When one bulb in your kitchen blows, why don't all the other lights in the house go out?

STUDENTS WILL BE ABLE TO

- tell series and parallel circuits apart
- use the rules for current and p.d. in each
- calculate total resistance in series
- explain why adding a parallel branch lowers the total resistance

WHY THIS LESSON, HERE

The series/parallel rules are taught as consequences of the Lesson 2–3 ideas: current is conserved (so it splits and rejoins) and energy per coulomb is shared (so p.d.s add in series).

PREPARATION AND EQUIPMENT

Per pair: cells, three identical lamps, two resistors, ammeters and voltmeters; or PhET. Mini whiteboards.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now	Retrieval: $V = IR$, wire length, meaning of volt.
6–18	Learn	Build two lamps in series, then in parallel; unscrew one lamp in each. Fill the rules table from observation.
18–28	Measure	Measure the numbers shown in the two labelled circuits. Check 'adds up' each time.
28–44	Try it	Worked example + Your turn, then Q1–Q6.
44–50	Exam corner	Question 7.



Hinge check. Q5: 6 Ω and 12 Ω in parallel. Anyone choosing 18 Ω is adding in parallel.

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
Current splits equally at every junction.	Use unequal branch currents (0.25 A, 0.15 A).
p.d. splits between parallel branches.	Each branch has the full supply p.d.
Adding a resistor always increases total resistance.	Checkout model: another route lowers it.

SUPPORT

Rules table on a card beside every question.

STRETCH

Mission 5 go-further box: $1/R = 1/R_1 + 1/R_2$ (beyond AQA, clearly labelled).

Homework: Mission 5 questions 1–5.

RESISTORS IN SERIES AND PARALLEL

AQA Combined RP 15; Physics RP 3; Part B; 50 minutes

BIG QUESTION Two identical resistors, three ways to connect them. Which arrangement lets the most current flow?

STUDENTS WILL BE ABLE TO

- measure the total resistance of resistors in series and in parallel
- compare results with $R_{\text{total}} = R_1 + R_2$
- explain the results using paths and current
- evaluate the measurements

WHY THIS LESSON, HERE

The second part of the resistance practical tests the Lesson 6 rules with measurements, and gives evaluation practice (specific error and improvement).

PREPARATION AND EQUIPMENT

Per group: low-voltage supply, switch, ammeter, voltmeter, two identical resistors (e.g. $10\ \Omega$), leads. Website practical page (Resistance, Part B) for reference.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now	Retrieval: series total, parallel rules.
6–12	Predict	Q1: rank the three arrangements. Record predictions on the board.
12–32	Practical	Four arrangements; V across the combination, I from the supply.
32–44	Analyse	Q3–Q6. Compare with predictions.
44–50	Exam corner	Question 7.



Hinge check. Before building: where does the voltmeter go for the parallel pair? (Across both.)

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
Measure V across one resistor only in parallel.	Across the combination.
Evaluation: 'human error'.	Name a specific error (lead resistance, resolution, heating) and a matching improvement.

SUPPORT

Circuit diagrams printed at each station.

STRETCH

Predict the result for three identical resistors in parallel and test it.

Homework: Workbook Revise it; Mission 5 question 6.

BIG QUESTION Every component has a 'fingerprint': the shape of its I-V graph. Could you identify a component from its graph alone?

STUDENTS WILL BE ABLE TO

- read an I-V graph, including negative values
- sketch and recognise the graphs for a fixed resistor, a filament lamp and a diode
- calculate the resistance at a point with $R = V \div I$
- explain the shape of each graph

WHY THIS LESSON, HERE

I-V graphs are taught as 'fingerprints' after students already know $R = V \div I$, ohmic behaviour and why heating raises resistance. The graph shapes follow from ideas they already have.

PREPARATION AND EQUIPMENT

Visualiser. Optional demo: lamp + variable supply with meters, to show resistance rising. Mini whiteboards for sketching.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0-6	Do now	Retrieval: ohmic, heating, R at a point.
6-20	Learn	Reading an I-V graph (both quadrants). Build the three shapes one at a time; students sketch each.
20-26	Explain	Lamp chain: current → heating → vibrating ions → collisions → R up → less steep.
26-44	Try it	Q1-Q5. Q3 (card-sort order) makes the causal chain explicit.
44-50	Exam corner	Question 6: sketch plus explanation.

 **Hinge check.** Q1: identify the three unlabelled graphs.

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
Resistance = gradient of the I-V graph.	Use $R = V \div I$ at a point; a curve's gradient does not give R.
The lamp graph flattens because the current 'runs out'.	Heating raises resistance.
Diode conducts both ways but less one way.	Very high resistance in reverse: almost zero current.

SUPPORT

Sketch templates with axes pre-drawn.

STRETCH

Mission 6 diode threshold question (≈ 0.6 V).

Homework: Mission 6 questions 1-2 and 4.

INVESTIGATING I-V CHARACTERISTICS

AQA Combined RP 16; Physics RP 4; 50 minutes

BIG QUESTION Can you produce the fingerprint graphs of a resistor, a lamp and a diode yourself?

STUDENTS WILL BE ABLE TO

- set up a circuit to vary the p.d. and measure the current
- take readings in both directions, safely
- plot an I-V graph with positive and negative values
- describe how the method changes for a diode

WHY THIS LESSON, HERE

Students now know what each graph should look like, so the practical tests predictions and focuses on method: varying p.d., reversing, safety and the diode's extra steps.

PREPARATION AND EQUIPMENT

Per group: variable low-voltage supply or supply + variable resistor, ammeter (and milliammeter), voltmeter, fixed resistor, 6 V filament lamp, diode + protective resistor (e.g. 100 Ω), leads. Website practical page (I-V characteristics) for reference.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now + safety	Retrieval. Lamp rating, hot lamp, protective resistor.
6–12	Set up	Check ammeter in series and voltmeter across the component only.
12–34	Practical	Resistor and lamp in both directions; diode with small steps.
34–44	Graph	Both components on one centred graph; sketch the diode.
44–50	Analyse	Q4–Q8; exam corner six-mark method as homework.



Hinge check. How do we get the negative readings? (Swap the supply connections; record as negative.)

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
Plotting reversed readings as positive.	Q8.
Voltmeter across the diode and protective resistor.	Across the diode only.

SUPPORT

Given target p.d.s in the table.

STRETCH

Explain why the lamp's resistance at 1 V is still larger than at 0.1 V.

Homework: Exam corner six-mark question. Mission 6 question 4.

THERMISTORS, LDRS AND SENSORS

AQA Combined 6.2.1.4, 6.2.2; Physics 4.2.1.4, 4.2.2; 50 minutes

BIG QUESTION How does a streetlight know it's getting dark, and how does a fire alarm know the room is hot?

STUDENTS WILL BE ABLE TO

- describe how a thermistor's resistance changes with temperature
- describe how an LDR's resistance changes with light intensity
- predict the current in a sensor circuit
- choose the right sensor for a job

WHY THIS LESSON, HERE

Thermistors and LDRs are taught as applications of 'lower total $R \rightarrow$ bigger current at fixed p.d.', so they revise $V = IR$ and series circuits while adding two new components.

PREPARATION AND EQUIPMENT

Thermistor and LDR with multimeter (resistance range); beaker of warm water; torch; mini whiteboards.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now	Retrieval: lamp graph, $V = IR$ direction, diode symbol.
6–18	Learn + demo	Measure R of the LDR (cover/torch) and thermistor (hand/warm water). Sketch the two graphs.
18–28	Sensor circuits	LDR in series; worked example and Your turn.
28–44	Try it	Q1–Q5.
44–50	Exam corner	Question 6.



Hinge check. Q5: which change increases the current through a thermistor?

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
Brighter light increases LDR resistance.	Both are 'more $\rightarrow$ less'.
Changing resistance changes the supply p.d.	The supply p.d. is fixed; the current changes.

SUPPORT

The 'more $\rightarrow$ less' key box as a card.

STRETCH

Explain why the p.d. across the fixed resistor rises as the LDR is lit (qualitative potential divider).

Homework: Mission 6 questions 3 and 5.

POWER AND ENERGY TRANSFER

AQA Combined 6.2.4.1–6.2.4.2; Physics 4.2.4.1–4.2.4.2; 50 minutes

BIG QUESTION Which transfers more energy: a 3 kW kettle boiling for 3 minutes, or a 10 W LED lamp left on for 5 hours?

STUDENTS WILL BE ABLE TO

- describe power as the energy transferred per second
- use $E = P t$, $P = V I$ and $P = I^2 R$ with the right units
- describe the energy transfers in everyday appliances
- choose the right equation for a question

WHY THIS LESSON, HERE

Power pulls together earlier quantities. Students choose between equations (the decision table) instead of memorising a list, and $P = I^2 R$ prepares the National Grid argument in Lesson 12.

PREPARATION AND EQUIPMENT

Appliance rating plates (photos or real). Calculators.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now	Retrieval: $E = Q V$, $Q = I t$, $V = I R$.
6–18	Learn	Power as J per s; appliance table; $E = P t$ worked example (unit conversions).
18–28	More power equations	$P = V I$ and $P = I^2 R$ worked examples; 'square the current first'.
28–44	Try it	Q1 is the big question; then Q2–Q6.
44–50	Exam corner	Question 7 (six marks).



Hinge check. Which equation? Show three sets of data and ask students to name the equation only.

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
$P = I^2 R$ calculated as $(I R)^2$ or $I \times 2 \times R$.	Square first, then multiply.
kW and minutes substituted directly.	Convert row in every frame.

SUPPORT

Decision table on a card.

STRETCH

Q6 (lamp current and resistance); cost of energy if the teacher adds kWh.

Homework: Mission 7 questions 1–4.

MAINS, SAFETY AND THE NATIONAL GRID

AQA Combined 6.2.3, 6.2.4.3; Physics 4.2.3, 4.2.4.3; 50 minutes

BIG QUESTION Pylon cables carry up to 400 000 V. Why so high, and why do we only get 230 V at the plug?

STUDENTS WILL BE ABLE TO

- describe the difference between ac and dc
- state the UK mains values: 230 V, 50 Hz
- explain how the earth wire and fuse protect you
- explain why the National Grid uses very high p.d.s

WHY THIS LESSON, HERE

Mains safety and the National Grid close the unit as one story, from power station to plug. The grid explanation uses $P = VI$ and $P = I^2 R$ from Lesson 11.

PREPARATION AND EQUIPMENT

Cut-away three-core cable or plug (no mains work by students). Transformer demo if available.

LESSON SEQUENCE

MIN	PHASE	TEACHER MOVES (WORKBOOK QUESTION NUMBERS IN THE LESSON)
0–6	Do now	Retrieval: $P = VI$, $P = I^2 R$, units.
6–16	ac/dc and mains	Traces or diagrams; 230 V, 50 Hz; cable colours and jobs.
16–26	Safety story	Live danger; earth + fuse sequence. Students order the events (Q3).
26–36	National Grid	Grid diagram; Q5 calculation shows the $\times 10 / \times 100$ effect.
36–50	Try it + exam corner	Q1–Q6, then exam corner Questions 7–8. Set the Unit review for home.



Hinge check. Q4 (Ava): is the live wire dangerous when switched off?

MISCONCEPTIONS TO EXPECT

STUDENTS MAY THINK...	ADDRESS IT BY...
Earth wire carries current all the time.	Only during a fault.
Step-up transformers make extra energy.	Power in = power out; p.d. up, current down.
Neutral is 'safe' and live only matters when on.	Live is at ~230 V whenever connected.

SUPPORT

Fault story as cut-out cards.

STRETCH

Higher-tier transformer question (Q6); explain why ac is needed for transformers.

Homework: Unit review (workbook), then Exam Zone on the companion website.