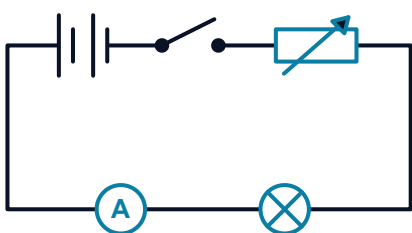



I-V characteristic of a filament lamp

A student finds the I-V characteristic of a filament lamp.


- 1** Connect the lamp in series with a power supply, a variable resistor and an ammeter.



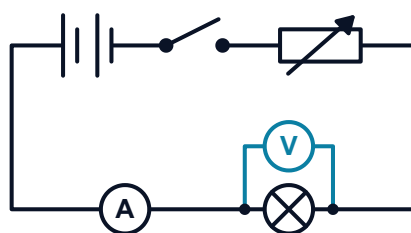
- 2** Connect a voltmeter in parallel with the lamp.



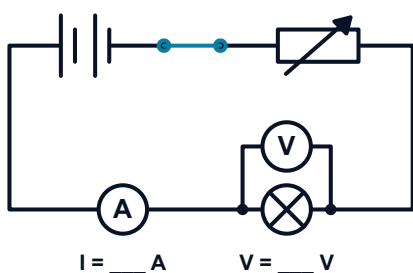
- 3** Record the current and the potential difference.



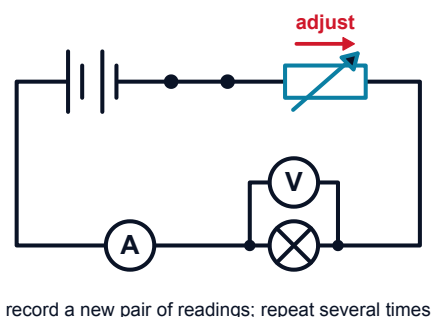- 4** Adjust the variable resistor and record a new pair of readings; do this several times.



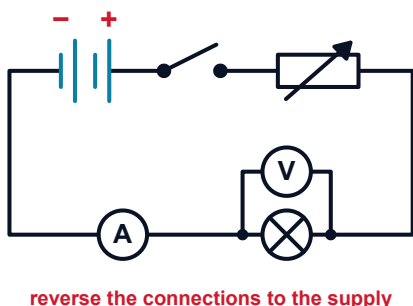- 5** Reverse the connections to the power supply and take the readings again.



- 6** Plot a graph of current against potential difference.

