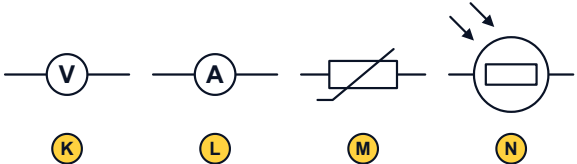
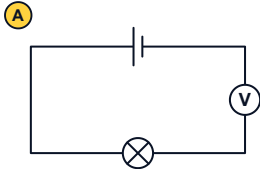
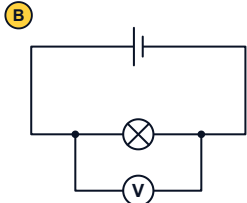
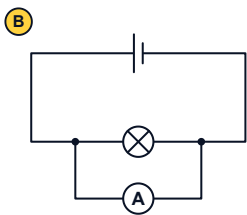


Standard circuit diagram symbols

Cover the answers. Answer each question out loud or on paper, then check. Tick the ones you know.

QUESTION	ANSWER	✓
1 Name the components labelled A to E in the diagram. 	A: open switch B: closed switch C: cell D: battery E: diode	☐
2 Name the components labelled F to J in the diagram. 	F: resistor G: variable resistor H: light-emitting diode (LED) I: lamp J: fuse	☐
3 Name the components labelled K to N in the diagram. 	K: voltmeter L: ammeter M: thermistor N: light-dependent resistor (LDR)	☐
4 State the function of a cell or battery.	To provide the potential difference that makes charge flow.	☐
5 State the difference between a cell and a battery.	A battery is two or more cells connected together.	☐
6 State the function of a diode.	To allow current in one direction only.	☐
7 State the function of a resistor.	To limit (reduce) the current in a circuit.	☐
8 State the function of a variable resistor.	To control the current by changing its resistance.	☐
9 State the function of an LED.	To emit light when current passes through it in the forward direction.	☐

QUESTION	ANSWER	✓
10 State the function of a fuse.	To melt and break the circuit if the current becomes too large.	☐
11 State the function of a voltmeter.	To measure potential difference.	☐
12 Which diagram, A or B, shows a voltmeter connected correctly across the lamp? Explain. A  B 	B. The voltmeter is in parallel with the lamp.	☐
13 State the function of an ammeter.	To measure current.	☐
14 Which diagram, A or B, shows an ammeter connected correctly to measure the current in the lamp? Explain. A  B 	A. The ammeter is in series with the lamp.	☐
15 State the function of a thermistor.	To sense temperature: its resistance changes with temperature.	☐
16 State the function of an LDR.	To sense light: its resistance changes with light intensity.	☐