

ELECTRIC CIRCUITS

LESSON 08 I-V GRAPHS

Every component has a 'fingerprint': the shape of its I-V graph. Could you identify a component from its graph alone?

IN THIS LESSON YOU WILL

- read an I-V graph, including negative values
- sketch and recognise the graphs for a fixed resistor, a filament lamp and a diode
- calculate the resistance at a point with $R = V \div I$
- explain the shape of each graph

ANSWER EDITION · FOR TEACHERS AND SELF-MARKING



NAME

CLASS

TEACHER

TARGET GRADE

HOW THIS BOOKLET WORKS

This is the booklet for **Lesson 8** of the Electric Circuits unit. It builds on the lessons before it; the “Do now” questions and the quick answers at the back help you check what you remember. Keep it: it is your classwork book *and* your revision guide.



DO NOW

Quick questions from earlier lessons. Remembering again is what makes it stick.



LEARN IT

The explanation, diagrams and worked examples. Read this again when you revise.



TRY IT

Practice that builds up: first with support, then on your own.



LAB

Record measurements from a virtual lab or a required practical.



EXAM CORNER

An AQA-style question with a tip on how the marks are given.



REVISE IT

Summary, cover-and-answer questions and an “I can” check to colour in.



Revising at home? (1) Read the Learn it pages. (2) Cover them and answer the “Cover the page” questions in Revise it. (3) Check with the quick answers at the back. (4) Do the matching mission on the companion website, which has more questions with answers.

THE ROUTE THROUGH THE UNIT · THIS LESSON IS HIGHLIGHTED

01 Complete circuits and symbols

03 Potential difference

05 Resistance of a wire **RP**

07 Resistors in series and parallel **RP**

09 Investigating I–V characteristics **RP**

11 Power and energy transfer

02 Current and charge

04 Resistance and $V = IR$

06 Series and parallel circuits

08 I–V graphs

I–V graphs of a fixed resistor, filament lamp and diode · Mission 6 · I–V characteristics

10 Thermistors, LDRs and sensors

12 Mains, safety and the National Grid

Companion website: panphy.app/gcsephy/year10phy/unit01 · missions, interactive equation triangles, required-practical pages and the Exam Zone.

BIG QUESTION Every component has a 'fingerprint': the shape of its I-V graph. Could you identify a component from its graph alone?

BY THE END YOU CAN

- read an I-V graph, including negative values
- sketch and recognise the graphs for a fixed resistor, a filament lamp and a diode
- calculate the resistance at a point with $R = V \div I$
- explain the shape of each graph

I-V characteristic

filament lamp

diode

LED

forward

reverse

ONLINE COMPANION

Mission 6 · I-V characteristics

Revision notes with graphs and 5 practice questions.

panphy.app/gcsephy/year10phy/unit01/lesson/iv-characteristics/



RETRIEVE

DO NOW

From earlier lessons. No notes!

1

What is an ohmic conductor?

Current $\propto$ p.d. at constant
temperature (constant
resistance).

2

Why does a metal's resistance increase when it gets hot?

Ions vibrate more, so
more collisions.

3

Calculate R for 4.0 V and 0.20 A.

20 Ω





READING COMPONENT FINGERPRINTS

On an **I-V graph**, current (I) goes up the side and p.d. (V) goes along the bottom.


Negative values mean the component is connected **the other way round**, so the current flows the other way.



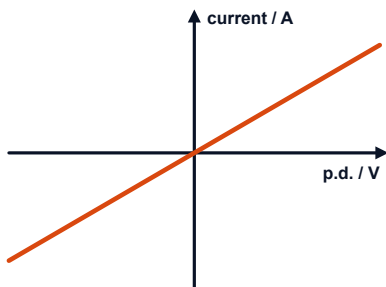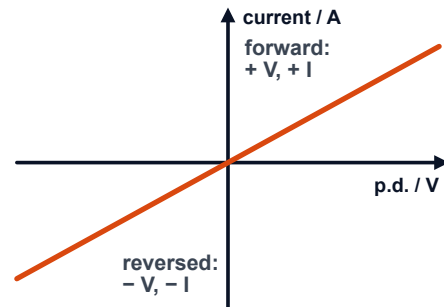
To find the resistance at any point, read V and I and use $R = V \div I$. Do not use the gradient.



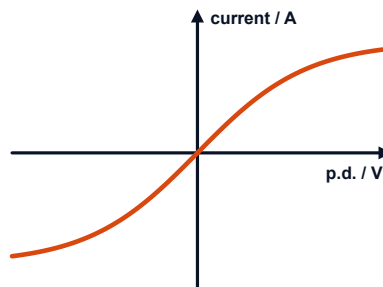Fixed resistor: straight line through the origin. Constant resistance (at constant temperature).



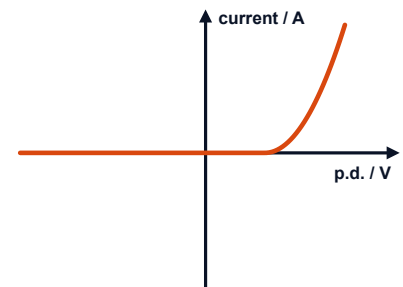Filament lamp: gets less steep. Resistance increases as the filament heats up.



Diode: current flows in one direction only. Very high resistance in reverse.


WHY DOES THE LAMP GRAPH BEND?

As the p.d. increases, the current increases. The current **heats the filament**. Hotter metal ions vibrate more, so electrons collide with them more often and the **resistance increases**. Each extra volt adds less current than the one before, so the graph gets less steep. It has the same shape for negative p.d. because the filament heats up whichever way the current flows.

DIODES AND LEDS

A **diode** lets current flow in one direction only: the way its triangle points. In the other direction its resistance is very high, so there is almost no current. Diodes protect circuits, for example if a battery is put in the wrong way round.



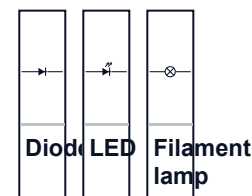
An **LED** (light-emitting diode) is a diode that gives out light when a current flows through it.






PRACTISE
TRY IT

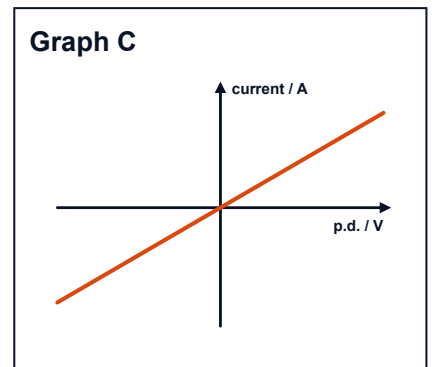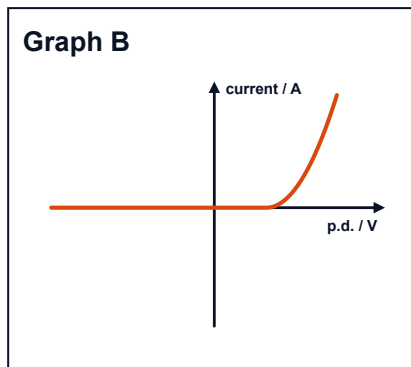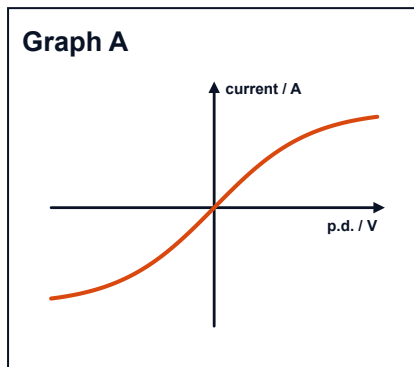- 1 Name the component that gives each graph.



A: filament lamp. B: diode. C: fixed resistor.

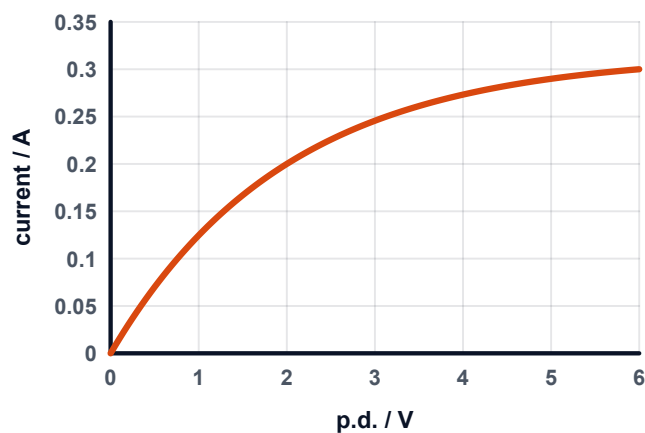- 2 This is the I–V graph for a filament lamp. (a) Read the current at 2.0 V and at 6.0 V. (b) Calculate the resistance at each p.d. (c) Explain why they are different.



(a) 0.20 A and 0.30 A. (b) $R = 2.0 \div 0.20 = 10 \Omega$; $R = 6.0 \div 0.30 = 20 \Omega$. (c) The larger current heats the filament more, so its resistance increases.

3 Number these statements 1–6 to explain the shape of a filament lamp's graph.

4 | The electrons collide with the ions more often

2 | The filament gets hotter

6 | So the I–V graph gets less steep

1 | The p.d. and the current increase

3 | The metal ions vibrate more

5 | The resistance of the filament increases

4 A component carries 0.10 A at 2.0 V and 0.15 A at 4.0 V. Is it an ohmic conductor? Show your working.

$R = 2.0 \div 0.10 = 20 \, \Omega$; $R = 4.0 \div 0.15 = 27 \, \Omega$. The resistance changes, so it is not ohmic.

5 What happens to the current through a diode when it is connected the other way round? Suggest one use for this.


There is (almost) no current: the diode has a very high resistance in reverse. Use:

protecting a circuit from a battery put in backwards, or making sure current flows only one way.



Get the marks: A sketch needs labelled axes and the right shape in both directions. The explanation needs cause $\rightarrow$ effect: current $\rightarrow$ heating $\rightarrow$ resistance.

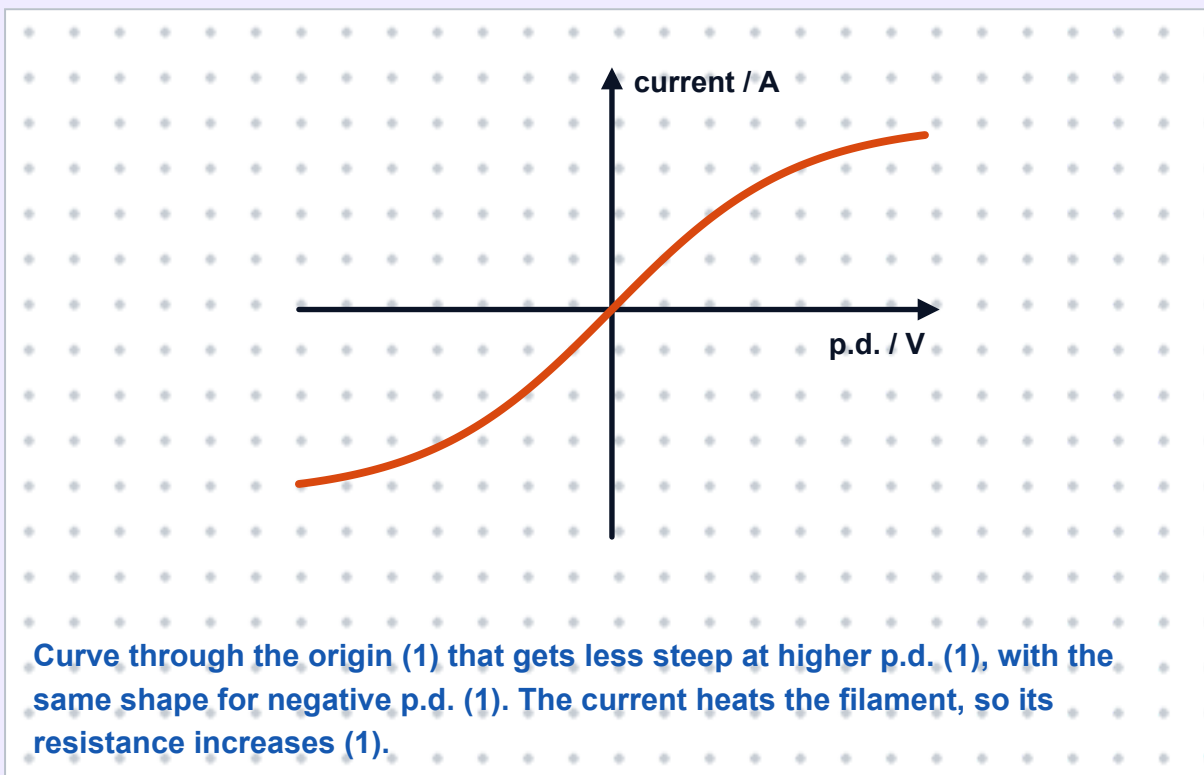- 6 Sketch the I–V graph of a filament lamp for positive and negative p.d. [4 marks]
Then explain its shape.



**SUMMARY**

- I–V graph: current up the side, p.d. along the bottom. Negative = connected the other way.
- Fixed resistor: straight line through the origin (constant R).
- Filament lamp: gets less steep; the filament heats up, so R increases.
- Diode: current in one direction only; very high resistance in reverse. An LED is a diode that gives out light.
- Resistance at a point: $R = V \div I$.

COVER THE PAGE AND ANSWER

1 Sketch the I–V graph for a fixed resistor.

2 Why does a filament lamp's resistance increase?

3 What does a diode do?

4 How do you find R at a point on an I–V graph?

I CAN...

read values from an I–V graph, including negative values



sketch the I–V graphs for a fixed resistor, lamp and diode



calculate resistance at a point



explain why the lamp graph curves



EQUATION TOOLKIT

The equations you have met so far. You will meet these one at a time. Learn each equation **in words** as well as symbols: your exams may or may not give you an equation sheet, and knowing them by heart makes every question faster.

$$Q = I t$$

Lesson 2

charge flow = current × time

C, A, s

Rearranged: $I = Q \div t$ · $t = Q \div I$

$$E = Q V$$

Lesson 3

energy transferred = charge ×
p.d.

J, C, V

Rearranged: $V = E \div Q$ · $Q = E \div V$

$$V = I R$$

Lesson 4

p.d. = current × resistance

V, A, Ω

Rearranged: $I = V \div R$ · $R = V \div I$

$$R_{\text{total}} = R_1 + R_2$$

Lesson 6

total resistance in series

Ω

Rearranged: (series only)

FOUR STEPS FOR EVERY CALCULATION

1

Write down what you know, with units.
Convert units first
(minutes → seconds,
kW → W, mA → A).

2

Write the equation you will use, in symbols.

3

Substitute the numbers, then rearrange if needed.

4




Give the answer with a unit. Ask: is it sensible?

CONVERT	HOW	EXAMPLE
minutes → seconds	× 60	3.0 min = 180 s
hours → seconds	× 3600	2.0 h = 7200 s
milliamps (mA) → amps (A)	÷ 1000	250 mA = 0.25 A
kilowatts (kW) → watts (W) · kilohms (k Ω) → ohms (Ω)	× 1000	2.2 kW = 2200 W
kilovolts (kV) → volts (V)	× 1000	400 kV = 400 000 V

EQUATION TRIANGLES: HELP WITH REARRANGING

- 1 Cover the quantity you want to find.
- 2 The two left **side by side**? **Multiply** them.
- 3 One **above** the other? **Divide** the top by the bottom.

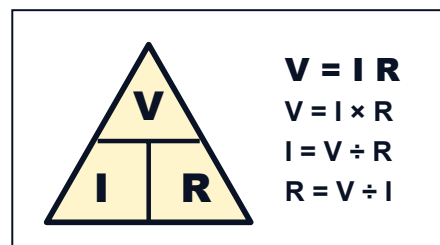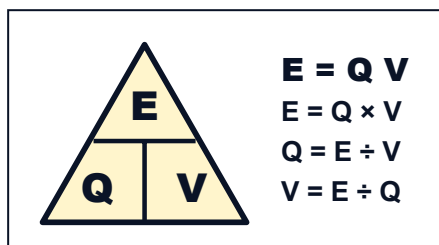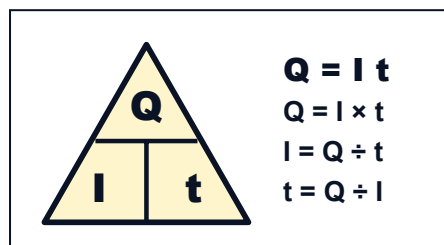Example: to find I from $Q = I t$, cover I . Q is above t , so $I = Q \div t$. Triangles only help with rearranging: you still need to learn each equation.



Interactive version: panphy.app/gcsephy/year10phy/unit01/equation-triangles.

REFERENCE

KEY WORDS FROM THIS LESSON

Learn the meaning and spelling. In exams, precise words earn marks: say “p.d. across” and “current through”.

Diode · Lets current flow in one direction only.

Filament lamp · A lamp with a thin metal filament; its resistance increases as it heats up.

I–V characteristic · A graph of current against p.d. for a component.

LED · Light-emitting diode: a diode that gives out light.

CHECK YOURSELF

QUICK ANSWERS

Answers to the “Do now” and “Cover the page” questions, so you can check yourself when revising. Answers to the longer questions are in your teacher's answer edition.

DO NOW

1. Current $\propto$ p.d. at constant temperature (constant resistance).
2. Ions vibrate more, so more collisions.
3. 20Ω

COVER THE PAGE

1. Straight line through the origin.
2. It gets hotter, so the ions vibrate more and there are more collisions.
3. Lets current flow in one direction only.
4. Read V and I ; $R = V \div I$.