

ELECTRIC CIRCUITS


LESSON 02 CURRENT AND CHARGE

Flick a switch and the lamp lights instantly, yet each electron drifts through the wire slower than a snail. How can both be true?

IN THIS LESSON YOU WILL

- describe current as the rate of flow of charge
- use $Q = I t$, with time in seconds
- explain why the current is the same everywhere in a single loop

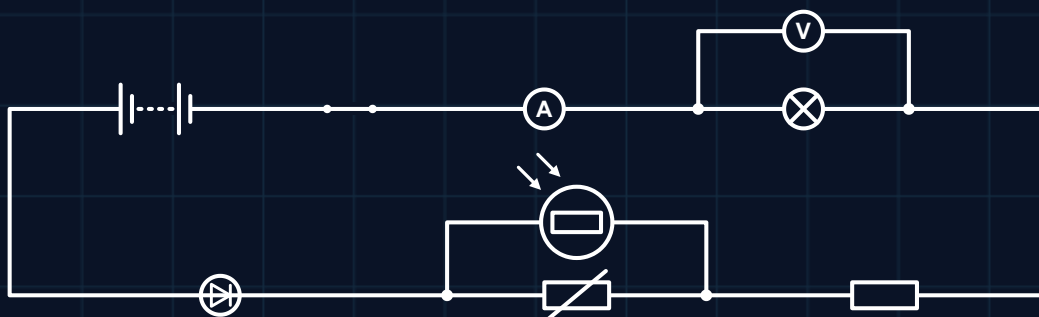ANSWER EDITION FOR TEACHERS AND SELF-MARKING



NAME

CLASS

TEACHER

TARGET GRADE

HOW THIS BOOKLET WORKS

This is the booklet for **Lesson 2** of the Electric Circuits unit. It builds on the lessons before it; the “Do now” questions and the quick answers at the back help you check what you remember. Keep it: it is your classwork book *and* your revision guide.



DO NOW

Quick questions from earlier lessons. Remembering again is what makes it stick.



LEARN IT

The explanation, diagrams and worked examples. Read this again when you revise.



TRY IT

Practice that builds up: first with support, then on your own.



LAB

Record measurements from a virtual lab or a required practical.



EXAM CORNER

An AQA-style question with a tip on how the marks are given.



REVISE IT

Summary, cover-and-answer questions and an “I can” check to colour in.



Revising at home? (1) Read the Learn it pages. (2) Cover them and answer the “Cover the page” questions in Revise it. (3) Check with the quick answers at the back. (4) Do the matching mission on the companion website, which has more questions with answers.

THE ROUTE THROUGH THE UNIT (THIS LESSON IS HIGHLIGHTED)

01 Complete circuits and symbols

03 Potential difference

05 Resistance of a wire RP

07 Resistors in series and parallel RP

09 Investigating I–V characteristics RP

11 Power and energy transfer

02 **Current and charge**

Current as a rate of flow of charge, $Q = I t$, current is not used up (Mission 2: Charge on the move)

04 Resistance and $V = I R$

06 Series and parallel circuits

08 I–V graphs

10 Thermistors, LDRs and sensors

12 Mains, safety and the National Grid

Companion website: panphy.app/gcsephy/year10phy/unit01: missions, interactive equation triangles, required-practical pages and the Exam Zone.

CURRENT AND CHARGE

AQA Combined 6.2.1.2; Physics 4.2.1.2; Virtual Lab 1

BIG QUESTION Flick a switch and the lamp lights instantly, yet each electron drifts through the wire slower than a snail. How can both be true?

BY THE END YOU CAN

- describe current as the rate of flow of charge
- use $Q = I t$, with time in seconds
- explain why the current is the same everywhere in a single loop

charge (C)

current (A)

coulomb

ampere

electron

conventional current

ONLINE COMPANION

Mission 2: Charge on the move

Revision notes and 5 practice questions with worked answers.

panphy.app/gcsephy/year10phy/unit01/lesson/charge-and-current/



RETRIEVE

DO NOW

From earlier lessons. No notes!

1

Draw the symbols for a cell and a lamp.

Cell: a long line and a shorter line (the long line is +). Lamp: circle with a cross.

2

How must an ammeter be connected?

In series (in the loop).

3


Give two reasons why a lamp in a circuit might not light.

Open switch; gap or loose wire; broken bulb; no cell.



EXPLAIN

WHAT IS FLOWING?

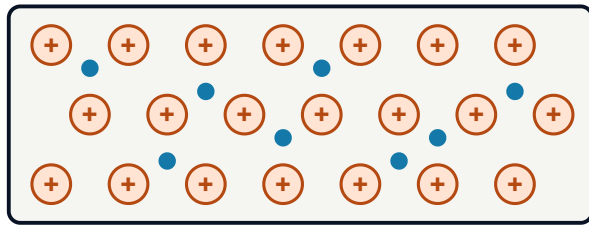

free electrons drift this way

Inside a metal wire: fixed positive ions (orange) and free electrons (blue).

Metals contain **free electrons**: tiny particles with a negative charge that can move between the atoms. The wires are full of them *before* you switch on.

The cell pushes on all of them at once, so the whole loop starts moving together, just like the bike chain. The lamp lights straight away, even though each electron only drifts along at less than a millimetre per second.

Charge is measured in **coulombs (C)**. One electron has a tiny charge: it takes about 6×10^{18} (six billion billion) electrons to make 1 C.

■ CURRENT IS A RATE

Current is the **rate of flow of charge**: how many coulombs pass a point *each second*.

THINK OF A TICKET BARRIER

Count the people going through a station barrier each second. The current is like the number of people *per second*, not the number of people in the station.

Where the model breaks: people can stop or change direction on their own; in a single loop all the charges move together.


! 1 ampere = 1 coulomb per second. A current of 0.5 A means 0.5 C of charge passes a point every second.

$$Q = I t$$

charge flow = current $\times$ time

Q in coulombs (C), I in amperes (A), t in seconds (s)

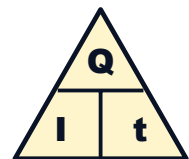Rearranged: $I = Q \div t$ and $t = Q \div I$



WORKED EXAMPLE

A current of 0.40 A flows for 3.0 minutes.
Calculate the charge that flows.

KNOW $I = 0.40 \text{ A}$, $t = 3.0 \times 60 = 180 \text{ s}$

EQUATION $Q = I t$

SUBSTITUTE $Q = 0.40 \times 180$

ANSWER $Q = 72 \text{ C}$

YOUR TURN

A current of 0.50 A flows for 4.0 minutes.
Calculate the charge that flows.


KNOW $I = 0.50 \text{ A}$, $t = 240 \text{ s}$

EQUATION $Q = I t$

SUBSTITUTE $Q = 0.50 \times 240$

ANSWER $Q = 120 \text{ C}$

CURRENT IS NOT USED UP

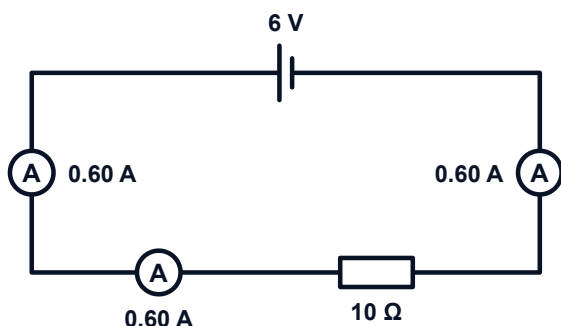

Three ammeters in one loop give the same reading.

In a single loop, the current is **the same at every point**. Charge is not destroyed in a component: it carries on round the circuit. What the component takes is **energy** (Lesson 3).




Charge goes round. Energy is transferred.

WHICH WAY DOES CURRENT FLOW?

Outside the cell, electrons flow from the **negative (-)** terminal to the **positive (+)** terminal.

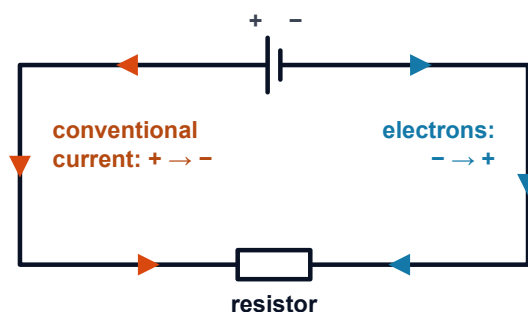But circuit diagrams show **conventional current**, from + to -. This was agreed before electrons were discovered. Both describe the same current, and exam diagrams use conventional current.



Orange: conventional current (+ to -). Blue: electron flow (- to +). Same current, opposite arrows.



PRACTISE
TRY IT

- 1 Complete the sentences using the word bank.

Current is the rate of flow of charge. It is measured in amperes (A) using an ammeter connected in series. Charge is measured in coulombs (C). A current of 2 A means 2 coulombs pass a point every second.

WORD BANK

charge

series

ammeter

second

amperes (A)

coulombs (C)

2

parallel

volts

- 2 A current of 0.60 A flows in a circuit. Which statement is correct? Tick **one** box.

- ☐ There is 0.60 C of charge in the circuit. ☒ 0.60 C of charge passes any point each second.
- ☐ The lamp uses up 0.60 C each second. ☐ The current is 0.60 A only near the cell.

- 3 **SUPPORTED** A current of 2.0 A flows for 30 s. Calculate the charge that flows.

EQUATION	$Q = I t$	
SUBSTITUTE	$Q = 2.0 \times 30$	
ANSWER	60 C	unit:

- 4 **SUPPORTED** A current of 0.30 A flows for 5.0 minutes. Calculate the charge. *Convert the time first!*

CONVERT	$t = 5.0 \times 60 = 300 \text{ s}$	
EQUATION	$Q = I t$	
SUBSTITUTE	$Q = 0.30 \times 300$	
ANSWER	90 C	unit:

- 5 **ON YOUR OWN** 36 C of charge passes through a lamp in 12 s. Calculate the current.

$$I = Q \div t = 36 \div 12 = 3.0 \text{ A}$$


- 6 **CHALLENGE** A phone charger supplies 0.80 A. How long does it take for 240 C to flow? Give your answer in seconds and in minutes.

$$t = Q \div I = 240 \div 0.80 = 300 \text{ s} = 5.0 \text{ minutes}$$

- 7 Predict the reading on A_2 . Explain why Mia is wrong.



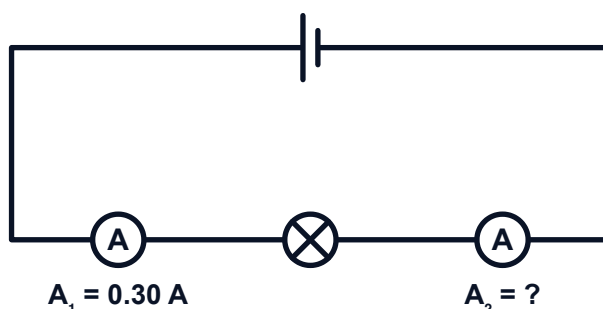The lamp uses up some current, so ammeter A_2 after the lamp will read less than A_1 .



$A_2 = 0.30 \text{ A}$. It is a single loop, so the current is the same everywhere. Charge is not used up: the lamp transfers energy, not charge.



INVESTIGATE

VIRTUAL LAB 1: IS CURRENT USED UP?

PhET Circuit Construction Kit: DC → Lab. Full steps: Virtual Labs worksheet pp. 3–6.

Build one loop with a **6 V battery** and a **10 Ω resistor**. Use the non-contact ammeter to measure the current at three places.

- 8 Record your readings.

Position	Current / A	Current with 20 Ω / A
Before the resistor	0.60	0.30
After the resistor	0.60	0.30
Next to the battery	0.60	0.30

- 9 What do your readings show? Use numbers in your answer.

All three readings are the same (0.60 A), so current is not used up. With 20 Ω the current halves (0.30 A) but is still the same everywhere.



Get the marks: Convert minutes to seconds before you substitute. The unit (C) is part of the answer.

- 10** A motor draws a current of 0.60 A for 5.0 minutes. Calculate the charge that flows through the motor. **[3 marks]**

EQUATION	$Q = I t$, with $t = 5.0 \times 60 = 300 \text{ s}$	
SUBSTITUTE	$Q = 0.60 \times 300$	
ANSWER	180 C	unit:

- 11** A student says the current leaving the motor is smaller than the current entering it. Explain why the student is wrong. **[2 marks]**

The motor is in a single loop, so the current is the same everywhere (1). Charge is not used up; the motor transfers energy (1).

**SUMMARY**

- Current is the **rate of flow of charge**. In metal wires the charges are free electrons.
- Charge: coulombs (C). Current: amperes (A). 1 A = 1 C per second.
- $Q = I t$, with t in seconds.
- In a single loop, current is the same everywhere: charge is not used up.
- Conventional current: + to -. Electrons: - to +.

COVER THE PAGE AND ANSWER

1 What is current?

3 Write the equation linking charge, current and time.

2 What is the unit of charge?

4 0.2 A flows into a lamp. What current flows out?

I CAN...

describe current as the rate of flow of charge



calculate charge, current or time using $Q = I t$



convert minutes to seconds before calculating



explain why current is not used up in a loop



EQUATION TOOLKIT

The equations you have met so far. You will meet these one at a time. Learn each equation **in words** as well as symbols: AQA gives you an equation sheet in the exam (it does not include $R_{\text{total}} = R_1 + R_2$), but knowing the equations by heart makes every question faster.

$$Q = I t$$

Lesson 2

charge flow = current $\times$ time

C, A, s

Rearranged: $I = Q \div t$ and $t = Q \div I$

FOUR STEPS FOR EVERY CALCULATION

1

Write down what you know, with units. Convert units first (minutes $\rightarrow$ seconds, kW $\rightarrow$ W, mA $\rightarrow$ A).

2

Write the equation you will use, in symbols.

3

Substitute the numbers, then rearrange if needed.

4


Give the answer with a unit. Ask: is it sensible?

CONVERT	HOW	EXAMPLE
minutes $\rightarrow$ seconds	$\times 60$	3.0 min = 180 s
hours $\rightarrow$ seconds	$\times 3600$	2.0 h = 7200 s
milliamps (mA) $\rightarrow$ amps (A)	$\div 1000$	250 mA = 0.25 A
kilowatts (kW) $\rightarrow$ watts (W); kilohms (k Ω) $\rightarrow$ ohms (Ω)	$\times 1000$	2.2 kW = 2200 W
kilovolts (kV) $\rightarrow$ volts (V)	$\times 1000$	400 kV = 400 000 V

EQUATION TRIANGLES: HELP WITH REARRANGING

- 1 Cover the quantity you want to find.
- 2 The two left **side by side**? **Multiply** them.
- 3 One **above** the other? **Divide** the top by the bottom.

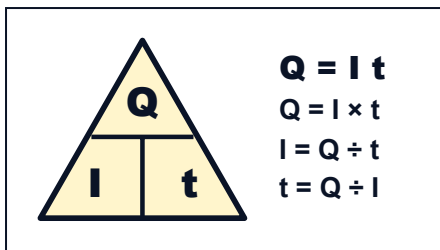Example: to find I from $Q = I t$, cover I . Q is above t , so $I = Q \div t$. Triangles only help with rearranging: you still need to learn each equation.



Interactive version: panphy.app/gcsephy/year10phy/unit01/equation-triangles.

REFERENCE

KEY WORDS FROM THIS LESSON

Learn the meaning and spelling. In exams, precise words earn marks: say “p.d. across” and “current through”.

Ampere (A): Unit of current. $1 \text{ A} = 1 \text{ C per second}$.

Charge (Q): Carried by particles such as electrons. Unit: coulomb (C).

Conventional current: The agreed direction of current: from + to –.

Electron: A tiny negatively charged particle. Free electrons carry the current in metals.

CHECK YOURSELF

QUICK ANSWERS

Answers to the “Do now” and “Cover the page” questions, so you can check yourself when revising. Answers to the longer questions are in your teacher's answer edition.

DO NOW

1. Cell: a long line and a shorter line (the long line is +). Lamp: circle with a cross.
2. In series (in the loop).
3. Open switch; gap or loose wire; broken bulb; no cell.

COVER THE PAGE

1. The rate of flow of charge.
2. Coulomb (C).
3. $Q = I t$
4. 0.2 A