PREP 1 · LESSONS 1–2

Complete circuits and current

Circuit symbols · ammeters · current as a flow of charge · Q = I t

SCORE / 10

Name _____ Class _____ Due _____

Do Now REMEMBER

From earlier lessons · 1 mark each

1 State the law of conservation of energy. DN 2 [1]

2 Define power. DN 31 [1]

3 Describe how a line of best fit should be drawn. DN 893 [1]

Key ideas LESSONS 1–2

Show your working

4 Look at this circuit.

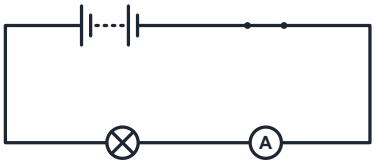

a The ammeter is connected in [series | parallel] with the lamp. [1]

b The switch is opened. Explain why the lamp goes out. [1]

c Describe the current at different points in this loop. [1]

5 A current of 0.40 A flows through a lamp for 60 s. Use Q = I t

Calculate the charge that flows through the lamp. [3]

6 State what is meant by electric current. [1]