PREP 5 · LESSONS 9–10

I–V investigations and sensors

Investigating I–V characteristics (required practical) · thermistors, LDRs and sensing circuits

SCORE / 10

Name _____ Class _____ Due _____

Do Now REMEMBER

From earlier lessons · 1 mark each

1 Explain why the resistance of a filament lamp increases with current. DN 102 [1]

2 State the function of a diode. DN 77 [1]

3 Describe the total resistance of two resistors connected in parallel. DN 636 [1]

Key ideas LESSONS 9–10

Show your working

4 A student finds the I–V characteristic of a lamp.

a Name the independent and dependent variables. [1]

b State why a variable resistor is included in the circuit. [1]

c Explain why the student reverses the connections to the lamp. [1]

5 As the temperature of a thermistor increases, its resistance | increases | decreases | stays the same | [1]

6 In the dark, the resistance of an LDR is | high | low | [1]

7 A thermistor is used in a circuit that switches on a fan when a room gets hot.

Explain what happens to the current in the thermistor as the room warms up. [2]