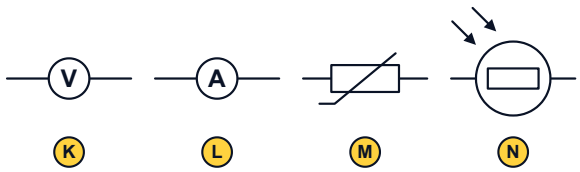
DO NOW, AO1 REVISION

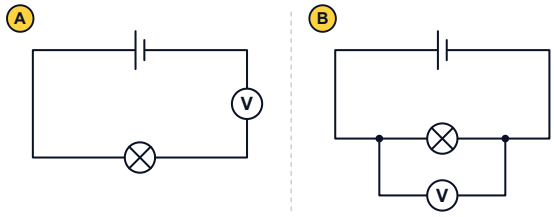
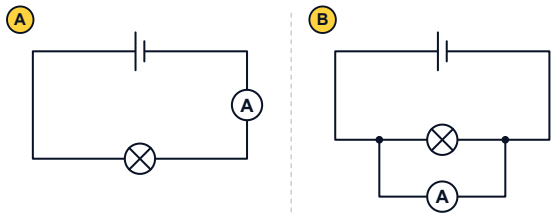
Standard circuit diagram symbols

Electricity
Paper 1, Combined and Separate
16 questions

Cover the answers. Answer each question out loud or on paper, then check. Tick the ones you know. Learn the 6 starred (★) questions first.

	QUESTION	ANSWER	✓
1 ★	**Name the components labelled A to E in the diagram.** 	A: open switch B: closed switch C: cell D: battery E: diode	☐
2 ★	**Name the components labelled F to J in the diagram.** 	F: resistor G: variable resistor H: light-emitting diode (LED) I: lamp J: fuse	☐
3 ★	**Name the components labelled K to N in the diagram.** 	K: voltmeter L: ammeter M: thermistor N: light-dependent resistor (LDR)	☐
4	**State the function of a cell or battery.**	To provide the potential difference that makes charge flow.	☐
5	**State the difference between a cell and a battery.**	A battery is two or more cells connected together.	☐
6 ★	**State the function of a diode.**	To allow current in one direction only.	☐
7	**State the function of a resistor.**	To limit (reduce) the current in a circuit.	☐
8	**State the function of a variable resistor.**	To control the current by changing its resistance.	☐

panphy.app, Do Now AO1 revision, © 2026 PanPhy Labs. All rights reserved.

	QUESTION	ANSWER	✓
9	**State the function of an LED.**	To emit light when current passes through it in the forward direction.	☐
10 ★	**State the function of a fuse.**	To melt and break the circuit if the current becomes too large.	☐
11	**State the function of a voltmeter.**	To measure potential difference.	☐
12 ★	**Which diagram, A or B, shows a voltmeter connected correctly across the lamp? Explain.** 	B. The voltmeter is in parallel with the lamp.	☐
13	**State the function of an ammeter.**	To measure current.	☐
14	**Which diagram, A or B, shows an ammeter connected correctly to measure the current in the lamp? Explain.** 	A. The ammeter is in series with the lamp.	☐
15	**State the function of a thermistor.**	To sense temperature: its resistance changes with temperature.	☐
16	**State the function of an LDR.**	To sense light: its resistance changes with light intensity.	☐

panphy.app, Do Now AO1 revision, © 2026 PanPhy Labs. All rights reserved.