
DO NOW, REQUIRED PRACTICAL

I–V characteristic of a filament lamp


Electricity
Paper 1, Combined and Separate
6 steps

A student finds the I–V characteristic of a filament lamp.

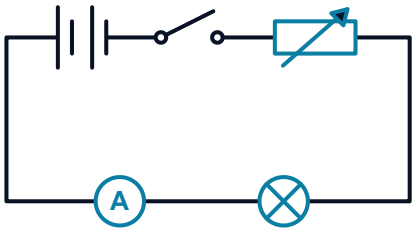
1 **Connect the lamp in series with a power supply, a variable resistor and an ammeter.**



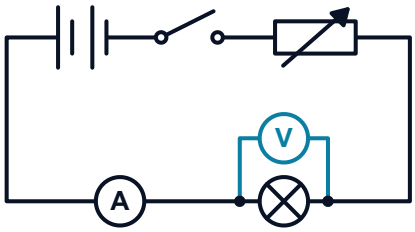2 **Connect a voltmeter in parallel with the lamp.**




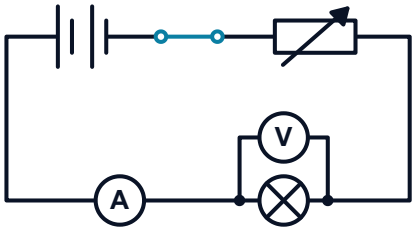3 **Record the current and the potential difference.**




I = ___ A V = ___ V

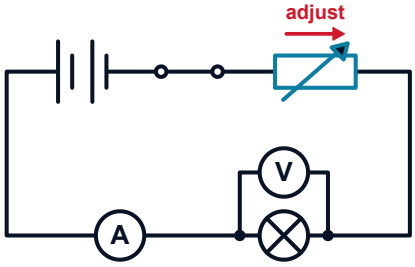4 **Adjust the variable resistor and record a new pair of readings; do this several times.**




record a new pair of readings; repeat several times

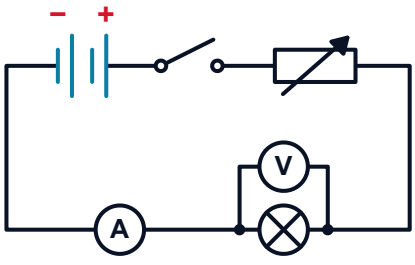5 **Reverse the connections to the power supply and take the readings again.**



reverse the connections to the supply

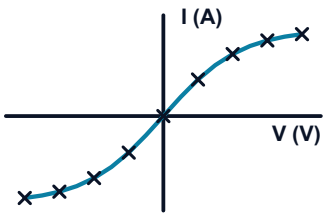6 **Plot a graph of current against potential difference.**



I against V, both directions

panphy.app, Do Now required practical, © 2026 PanPhy Labs. All rights reserved.